Kinetic Energy Lab Sequence

- 1. Find a generator.
- 2. Find a way to turn, crank, etc your generator.
- Turn the generator and measure open circuit voltage (OCV).
 3.1.Multimeter in DC volts (for DC motor) or AC volts (for stepper)
- 4. Turn the generator and measure short circuit current (SCC).
 - 4.1.Multimeter in DC current (for DC motor) or AC current (for stepper)
 - 4.2.Note, the multimeter works differently in current vs other modes. In current mode it is a series part of the circuit, so when we use it to measure current here we are "short circuiting" the current.
- 5. Calculate the upper limit power for your generator,
 - 5.1. Multiply SCC in amps x OCV in volts to get power in watts
 - 5.2. This will be an outside case: the highest voltage your generator will generate is in OCV; the highest current in SCC; any real-world application will be some intermediate value for both.
- 6. Connect an LED to your generator.
 - 6.1.Does it light up? Check the polarity. For a stepper, LEDs in opposite phases can light up, because the steppers produce AC. You might be able to see this - if your smart phone has a slow-motion video feature, record the LEDs and you may see alternate flashing.
 - 6.2. Does it blow up? Add resistors.
 - 6.3. How many in series can you light up?
- 7. Rectify the output.
 - 7.1.Use the bridge rectifier component so that your stepper's AC is DC; or so your DC motor outputs the same polarity no matter which way it is turned.
 - 7.2.Add an LED circuit after the rectifier. Make sure to use an appropriate resistor from now on.
- 8. Smooth the output.
 - 8.1.Add a capacitor after the rectifier. Try various sizes from 1uF to 10,000uF or even bigger.
- 9. Add a switch.
 - 9.1.If you put a switch or button between the LED and the capacitor, you can charge the capacitor and then discharge it (lighting the LED) when you choose.
- 10. Build the VU meter circuit.
 - 10.1.Use a series of LEDs and diodes to make a circuit that progressively lights up the higher the voltage is.